

# 7-Segment Display using Flysky Transmitter

B603 Lab

Indian Institute of Technology, Hyderabad.



December 1, 2021

# Components

- 1 Flysky Receiver and Transmitter
- 2 ESP32
- 3 7 Segment Display

# Pinout Diagram of 7-Segment Display

7-SEGMENT-DISPLAY CA

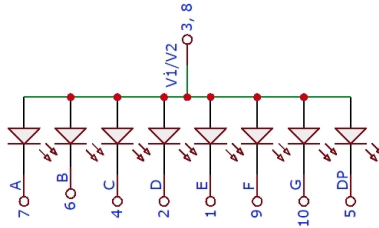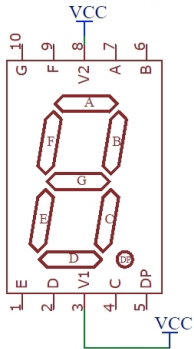

## Wiring Diagram: Flysky-Rx and ESP32

Flysky-Rx pin	ESP32 pin
Channel 2	Pin-14
Channel 4	Pin-15
GND	GND
Vin	5v

## Wiring Diagram: 7-Segment Display and ESP32

<b>7-Segment pin</b>	<b>ESP32 pin</b>
Pin 1	P-19
Pin 2	P-17
Pin 4	P-18
Pin 6	P-18
Pin 7	P-16
Pin 8	3.3V
Pin 9	P-19

## Wiring Diagram: Flysky-Rx and Arduino

<b>Flysky-Rx pin</b>	<b>Arduino pin</b>
Channel 2	Pin-10
Channel 4	Pin-11
GND	GND
Vin	5v

# Wiring Diagram: 7-Segment Display and Arduino

7-Segment pin	Arduino pin
Pin 1	P-2
Pin 2	P-3
Pin 4	P-4
Pin 6	P-4
Pin 7	P-5
Pin 8	3.3V
Pin 9	P-2

## Binding Tx. and Rx.

- Check the reference number of the receiver and transmitter. If they are same, then no need of binding.
- If the reference numbers are not same then binding of Rx and Tx is needed.



## Binding Tx. and Rx.



Figure: Flysky Receiver

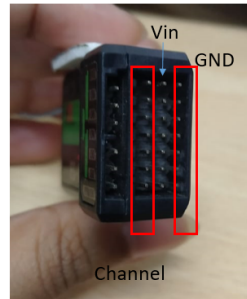


Figure: Flysky Receiver

## Binding Tx. and Rx.

- Short the GND and CHANNEL pin of B/VCC of the receiver.
- Connect Vin pin with 5V pin of ESP32 and GND pin to GND pin of ESP32.
- Press the bind key of the transmitter.

# Code

- Flash the code from arduino IDE to ESP32.  
[https://github.com/JayatiD93/7SegmentDisplay\\_ESP32/blob/main/flysky\\_7Segment.ino](https://github.com/JayatiD93/7SegmentDisplay_ESP32/blob/main/flysky_7Segment.ino)